

Exponential Current DAC

By: Monish Reddy Kalapureddy (z5364797),
Ibrahim Ali Harbi (z5078105)

Objective:

To design a current-output digital-to-analog converter (iDAC) with an exponential code-current relationship. This is represented with the equation:

$$i_{OUT, tgt}(B) = I_{LSB} \cdot \alpha_R^{B/(2^N - 1)}$$

Where, based on the design constraints,
 $I_{LSB} = 10\mu A$ and $\alpha_R = 20$. $N = 3$ was chosen to minimise complexity of the design, hence $B \in [0, 7]$, $B = B_2 B_1 B_0$.

Furthermore, the performance measure we are trying to maximise is M, which is:

$$M = \frac{2^N}{P_S \cdot |DNL| \cdot t_S \cdot |\epsilon_{Scale}| \cdot \epsilon_{out} \cdot |\Delta I_{LSB}| \cdot A_{LO} \cdot V_{L, min}}$$

To maximise M, all the variables in the denominator will be minimised to obtain the maximum value. Since the worst-case values are expected for M as input, the maximum value of the design changes/

simulations will be used to determine the performance quality of the iDAC.

Circuit topology:

The proposed current-steering iDAC is implemented using a 3-to-8 digital demultiplexer, level shifters for domain translation, and a current-mirror-based analog output stage. This topology provides accurate current output for each value of B while remaining compatible with standard CMOS processes.

Fig 2: Test bench schematic with the biasing loads and voltages.

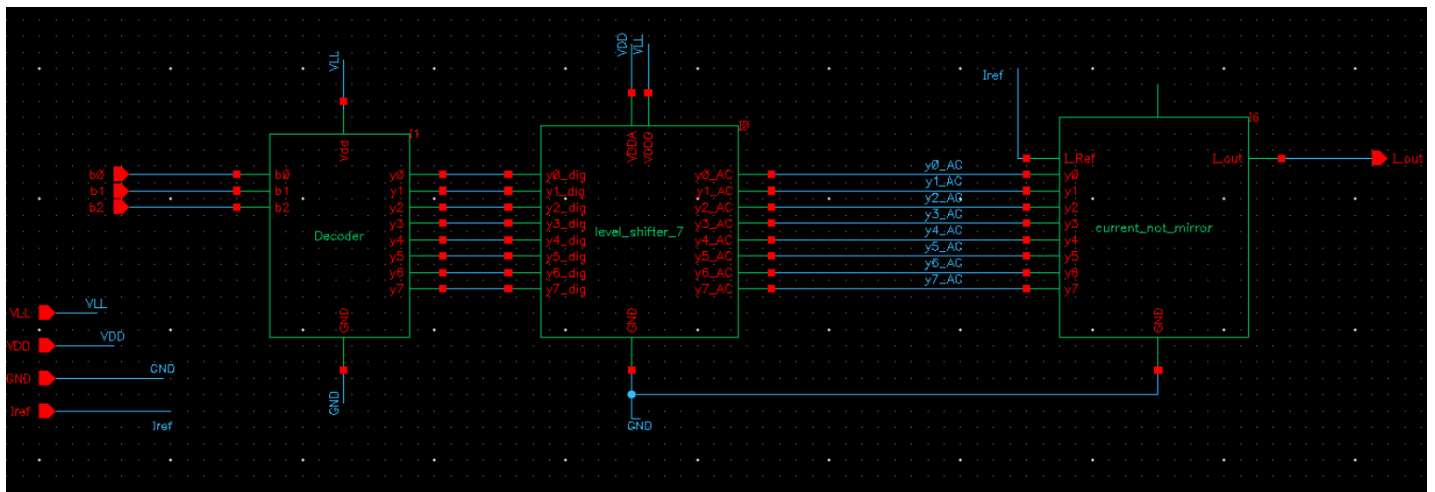
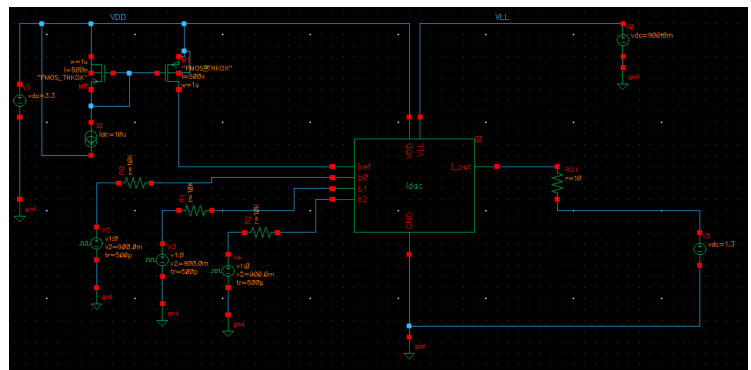


Fig 1: The topology of the circuit consisting of the digital block (decoder and the level shifter) and analog block (current mirror within which is are switches and buffer)

1. Digital Circuit:

3-to-8 demultiplexer:

The IDAC employs a 3-bit binary input that is converted to a one-hot control vector using a CMOS 3-to-8 decoder. This approach enables thermometer-coded selection, where only a single output line is active at any given time. Thermometer coding is preferred in mixed-signal CMOS design because it guarantees monotonicity and

significantly reduces digital switching glitches compared to binary-weighted implementations.

As a result, the chosen transistor type was a VTG CMOS structure, as it is especially suited for our application due to its maximum supply voltage of 0.9V, and is generally useful for fast switching speeds (especially useful to reduce settling time) and low power consumption (reduces P_S).

Furthermore, they also function at lower widths and

lengths, minimising the area of the layout which is especially important for the performance measure, especially in comparison to the Thick-Oxide CMOS that will be used in the analog stages to compensate for the 3.3V power supply application.

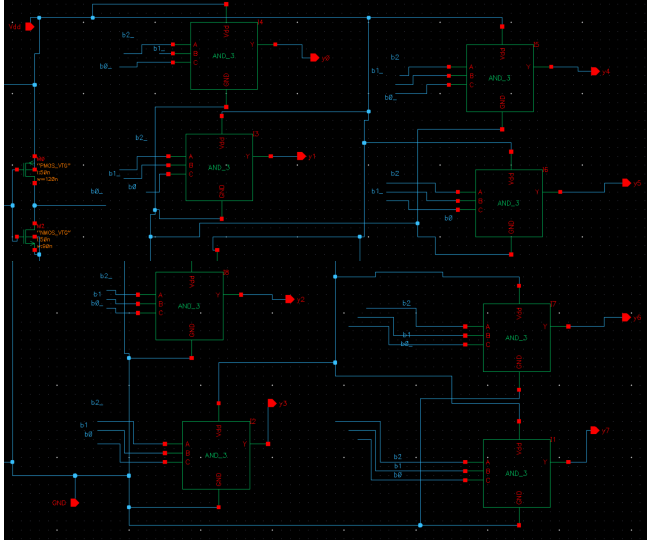


Fig 3: The logic blocks of the demultiplexer composed of a single AND gate, utilising the logic expression to encode the input information

Hence, the function of the demultiplexer is to represent the 8 unique values of B as a unique signal, which will later produce their own individual currents to represent the value as an AC current.

Hence, to represent the logic of the input 3 bit voltages to 8 separate voltages of 0.9V, the following truth table was used to design the multiplexer:

| B_2 | B_1 | B_0 | B | Logic equation |
|-------|-------|-------|-----|--|
| 0 | 0 | 0 | 0 | $\overline{B_2} \overline{B_1} \overline{B_0}$ |
| 0 | 0 | 1 | 1 | $\overline{B_2} \overline{B_1} B_0$ |
| 0 | 1 | 0 | 2 | $\overline{B_2} B_1 \overline{B_0}$ |
| 0 | 1 | 1 | 3 | $\overline{B_2} B_1 B_0$ |
| 1 | 0 | 0 | 4 | $B_2 \overline{B_1} \overline{B_0}$ |
| 1 | 0 | 1 | 5 | $B_2 \overline{B_1} B_0$ |
| 1 | 1 | 0 | 6 | $B_2 B_1 \overline{B_0}$ |

| | | | | |
|---|---|---|---|---------------|
| 1 | 1 | 1 | 7 | $B_2 B_1 B_0$ |
|---|---|---|---|---------------|

Table 1: Logic implementation of the demultiplexer block

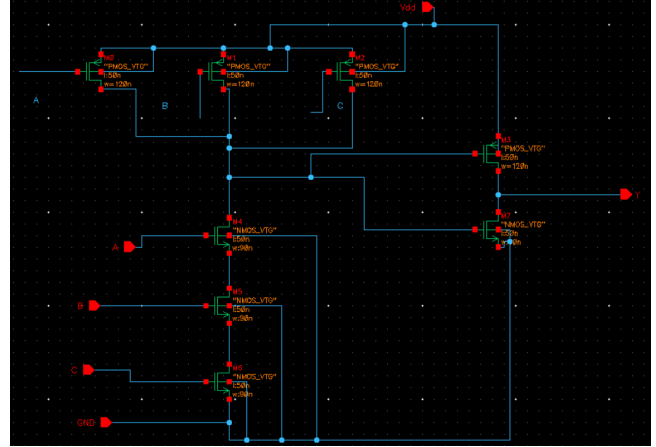


Fig 4: Schematic of the AND gate with dimensions

For the 3-input NAND gate, the widths and lengths were the lowest that this CMOS technology can handle which is

$$W_{NMOS} = 90n, W_{PNOS} = 120nm,$$

$$L_{NMOS} = L_{PNOS} = 50nm$$

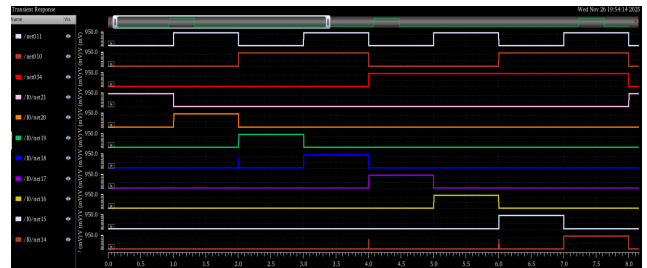


Fig 5: Transient simulation showing the demultiplexing of signal

Level Shifter:

To use the digital signal in the analog circuit, the voltage needs to be amplified to 3.3V, to ensure the switches in the analog circuit are in saturation mode. There were 2 main architectures considered for this function: a differential amplifier with a reference voltage or a level shifter circuit.

A level shifter is preferred over a voltage amplifier for interfacing the digital decoder with the analog switching network because unlike an amplifier, which produces a scaled analog output and cannot guarantee rail-to-rail swing due to headroom and bandwidth limitations, a level shifter generates well-defined digital "0" and "1" levels at the required higher supply voltage, ensuring that the MOS switches in the iDAC are fully enhanced and operate with minimal on-resistance.

Level shifters also consume negligible static power, occupy far less silicon area, and avoid stability and compensation issues inherent in amplifiers. Additionally, they inherently protect low-voltage transistors from gate-oxide overstress when crossing voltage domains. For these reasons, a level shifter offers a simpler, more reliable, and more power-efficient solution for digital-to-analog domain interfacing in CMOS iDAC designs.

The widths and lengths of the thick-oxide transistor (the analog conversion component of the level shifter) must be at least 3 times that of the digital inverters used in the previous blocks. Furthermore, the output resistance of this component must be significantly lower than that of the current mirror, represented by $R_{on} = L/(k_{\lambda} I_D)$, hence a larger length for the thick-oxide CMOS. Finally, the NMOS pull-down network is typically sized larger than the PMOS pull-up devices to ensure reliable switching when translating from a low-voltage digital domain to a higher-voltage analog domain to ensure rapid discharging. Through experimentation, a width of $20\mu m$ was optimal in ensuring a stable digital output scale for the analog component.

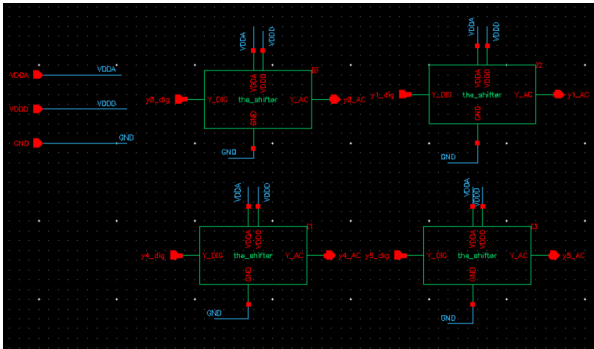


Fig 6: The 7 level shifter for each of the digital number signal lines

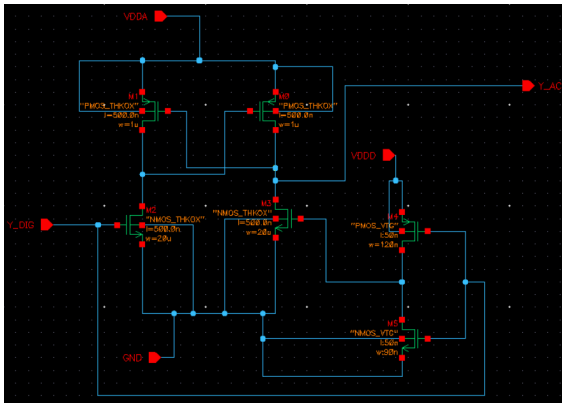


Fig 7: Transistor widths and lengths of the level shifter, with a large pull-down network width to ensure safe amplification

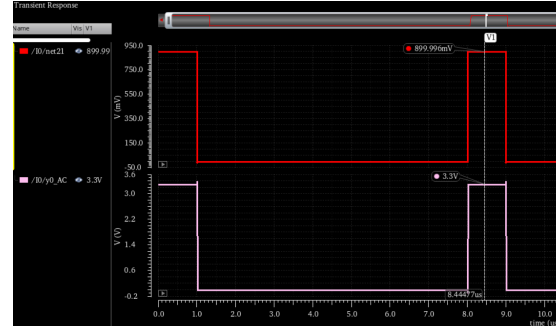


Fig 8: The digital input ($V = 0.9V$) and amplified output ($V = 3.3V$) of the level shifter

2. Analog Circuit

Current mirror:

A current mirror is the most suitable structure for implementing an iDAC because it provides accurate and repeatable current generation based on transistor geometry ratios rather than absolute device values, which are poorly controlled in CMOS.

This component is the first to use the source current reference, which has been decided to be $10\mu A$, which is the LSB current.

The PMOS in the test bench is set to be of with a width of $2\mu m$, the same as that of the output PMOS of the level shifter. An NMOS network is used within the current mirror to ensure the current is correctly pulled down and to prevent interference from the output voltages in biasing the mirror. Since the currents in each of the current mirror channels (1 channel per value of B) are larger than $10mA$, the calculated widths of the NMOS and the implemented widths are as shown below:

| $I_{out, expected}$ [mA] | $W_{NMOS, theoretical}$ [μm] | $W_{NMOS, real}$ [μm] |
|--------------------------|-------------------------------------|------------------------------|
| 10.000 | 1.000 | 1.000 |
| 15.341 | 1.534 | 0.747 |
| 23.535 | 2.354 | 1.280 |
| 36.106 | 3.611 | 2.000 |
| 55.392 | 5.539 | 3.200 |
| 84.978 | 8.498 | 5.100 |
| 130.367 | 13.037 | 7.500 |
| 200.000 | 20.000 | 12.000 |

Table 9: Calculated based on the ratio of the current-replicating NMOS of width $1\mu m$, which has a current of $10mA$ to the amplified current.

A current mirror is preferred over an amplifier for IDAC implementation because it directly replicates and scales currents with minimal logic delay and far greater architectural flexibility. Since a current mirror operates purely through transistor biasing, the output current responds immediately to digital switching of the unit branches, avoiding the settling-time overhead, compensation requirements, and bandwidth limitations inherent in amplifiers. This allows faster, more deterministic switching and reduces latency through the DAC path.

Despite its advantages, a current-mirror-based IDAC has several limitations compared to amplifier-based approaches. Its accuracy depends strongly on device matching and layout quality, with variations in threshold voltage, mobility, and channel-length modulation directly affecting linearity. The finite output resistance of mirror devices also restricts output compliance, causing current errors as the output voltage varies, whereas amplifiers can use feedback to maintain accurate current over a wider operating range. Hence, considering these options, the current mirror was chosen primarily due to its flexibility in prototyping, over a potentially more power drawing, wider layout area amplifier design which works better for linear DAC's due to its linear growth and direct regular interval amplification.

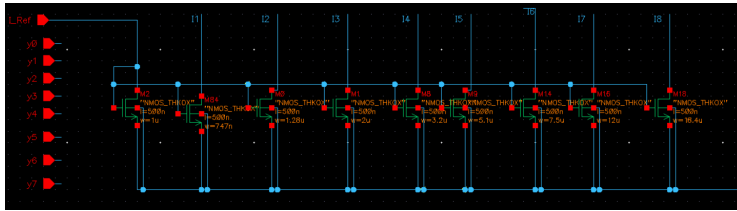


Fig 10: Schematic of the current with transistor dimensions represented in **Table 2**.

Switching:

The initial prototypes started with the implementation of a transmission gate, but the key drawback was the introduction of V_{DD} back into the current mirror conflicting with the load voltages and working against NMOS pull-down network current mirror. Hence a simple NMOS switching network was used.


Increasing transistor length to $1\mu m$ improved matching, output dependence, and enhanced analog accuracy, but it slows switching due to increased on-resistance and capacitance. This was a compromise that could be made due to the highly optimised digital topology, ensuring a stable current output through the switches without a significant settling time or propagation delay.

The widths of all of the switches were maintained to be a constant of $8\mu m$ to ensure the channel is large enough for even the highest current of the current mirror to flow through.

A small capacitor of $1nF$ was integrated at the end as a filter to minimise the impact of the load voltages and reduce the large spikes and sudden changes that were prevalent in multiple initial versions of the design. A parametric sweep was done to ensure the impact of the capacitor was minimal on the switching speed, but is a temporary solution for a full implementation of a buffer.

To achieve this, an **inverter buffer** or an **output cascoded current mirror** is required, increasing the small-signal output resistance while reducing current variation with load compliance voltage.

Fig 11: The NMOS switching network with a buffer capacitor to protect the mirror from load voltages and minimise current spikes

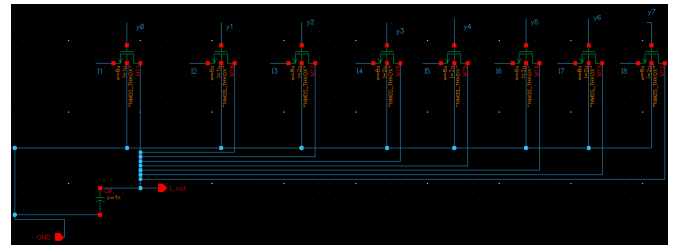

Circuit simulations:

Transient simulation:

Fig 12: At $V_L = 2.5V$ and $R_L = 0\Omega$


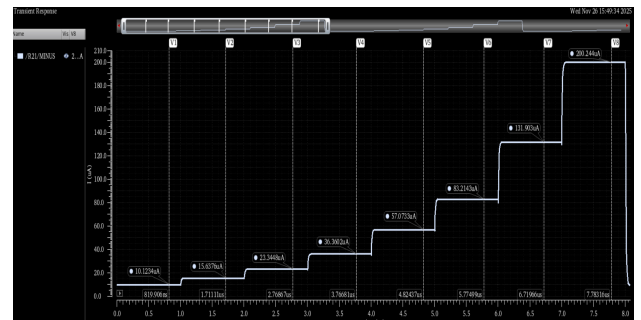


Fig 13: At $V_L = 3.3V$ and $R_L = 10k\Omega$

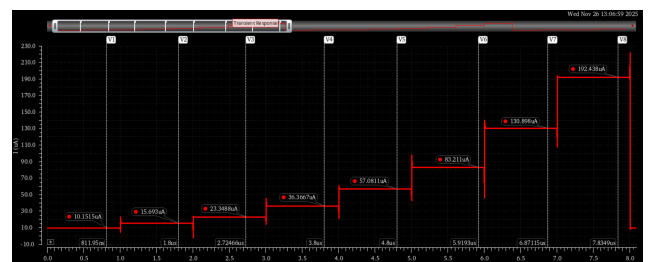

| i_out_measured [μA] | I_out_cmp [μA] | DNL | ΔI_cmp |
|---------------------|----------------|---------------|-------------|
| 10.1234 | 10.1234 | | 2.084494626 |
| 15.6376 | 15.50609914 | 0.02443028162 | 3.192838407 |
| 23.3448 | 23.75082588 | 0.06519642781 | 4.890498142 |
| 36.36 | 36.37934496 | 0.03061965635 | 7.490818208 |
| 57.0733 | 55.72255663 | 0.07083044727 | 11.47375089 |
| 83.21 | 85.35072087 | 0.1178427462 | 17.57444326 |
| 131.903 | 130.7324357 | 0.07296518339 | 26.91892641 |
| 200.244 | 200.244 | 0.0168398495 | 41.23195189 |

Range scale error: 0.01098
LSB offset: 0.123μA

The calculation of relative output current variation due to output voltage using the table below:

| V _I = 2.5V | V _I = 1.3V | V _I = 3.3V | |
|--------------------------------|--------------------------------|--------------------------------|------------------|
| R = 0 | R = 0 | R = 0 | |
| I _{out_measured} [μA] | I _{out_measured} [μA] | I _{out_measured} [μA] | ε _{out} |
| 10.1491 | 9.56 | 10.1518 | 0.058311 |
| 15.6894 | 14.74 | 15.7 | 0.061188 |
| 23.3500 | 22.0054 | 23.35 | 0.057585 |
| 36.3600 | 34.33 | 36.37 | 0.056106 |
| 57.0737 | 54.0312 | 57.093 | 0.053646 |
| 83.2100 | 79.002 | 83.25 | 0.051052 |
| 131.9000 | 125.735 | 131.97 | 0.047271 |
| 200.2400 | 191.62 | 200.349 | 0.043593 |

The calculated area of the layout is specified below:

| | |
|-------------------------------------|---------|
| A(and gate) [μm²] | 0.042 |
| A(decoder) [μm²] | 0.36750 |
| A(shifter) [μm²] | 168.084 |
| A(mirror) [μm²] | 25.6135 |
| A(switches) [μm²] | 128.000 |
| A(total) | 322.065 |

Hence, this leads to:

| 2 ^N | P _{sup} [mW] | DNL(max) | t _S [μs] (max) | ε _{scale} |
|------------------|-----------------------|------------------------------------|------------------------------|--------------------|
| 8 | 0.00147981 | 0.1178 | 0.000051730 | 0.01098445186 |
| ε _{out} | ΔLSB [μA] | A _{LO} [μm ²] | V _{L,min} [V] | M |
| 0.061188 | 0.123000 | 16882.6 | 1.3 | 488773457.5 |

Hence, under these conditions, the worst-case calculated M is:

$$4.888 \times 10^8 (mW \cdot \mu s \cdot \mu A \cdot \mu m^2 \cdot V)^{-1}$$

Finally when the load resistance is 10kΩ:

| I _{out_measured} [μA], R=10kΩ | Δi _{out,cmp} , R = 10kΩ |
|---|----------------------------------|
| 10.152 | 2.090 |
| 15.693 | 3.182 |
| 23.348 | 4.845 |
| 36.367 | 7.376 |
| 57.081 | 11.229 |
| 83.211 | 17.096 |

| | |
|---------|--------|
| 130.898 | 26.027 |
| 192.438 | 39.625 |

Appendix:

Other design constraints include:

| Parameter | Value |
|---|---------------|
| Power supply V _{DD} | 3.3 V |
| Power supply V _{LL} | 0.9 V |
| Bias current | 10μA |
| Bias voltage | Unused |
| Logic high V _H | 0.9 V |
| Logic low V _L | 0 V |
| Load resistance R _L | 0kΩ, 10kΩ |
| Minimum load voltage R _L | Fixed to 1.3V |
| Source Resistance R _S | 10kΩ |
| Maximum dynamic non-linearity DNL(B) _{max} | ≤ 1 |

Where:

P_S = iDAC power consumption [mW]

DNL = differential non-linearly [unitless] - measure of the deviation between i_{OUT,tgt}(B) and

i_{OUT,meas}(B)

t_S = settling time [μs] - time it takes to go from

i_{OUT}(0) to i_{OUT}(B)

ε_{Scale} = range scale error [unitless] - deviation of the range of output from the expected output range characterised by α_R

ε_{Out} = relative output current variation due to output voltage [unitless]

ΔI_{LSB} = least-significant bit error [μA] - difference between the expected LSB current and the actual LSB current

A_{LO} = Estimated area layout [μm²]

V_{L,min} = lowest load voltage [V]

Current values for fig 12 and 13:

| I_out_measured (microA) R=10k | I_out_measured (microA) R=0 |
|--|--|
| 10.1515 | 10.1491 |
| 15.6930 | 15.6894 |
| 23.3480 | 23.3500 |
| 36.3667 | 36.3600 |
| 57.0811 | 57.0737 |
| 83.2110 | 83.2100 |
| 130.8980 | 131.9000 |
| 192.4380 | 200.2400 |